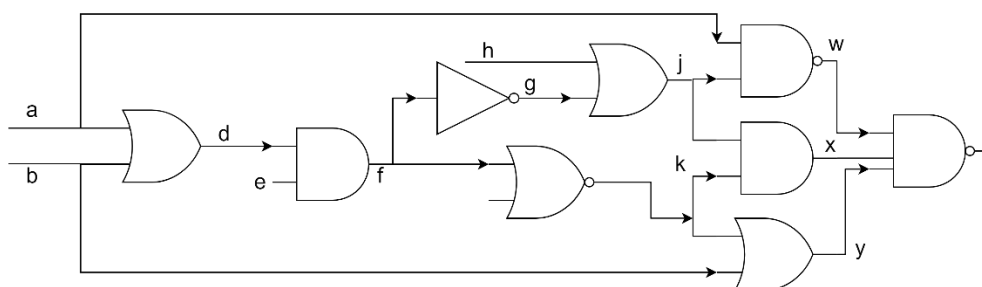


## DFT Assignment-2


### Instructions:

- Consider the Combinational Logic and write a Verilog/VHDL gate level code and testbench.
- Generate a table for all the test vectors and output patterns for all the stuck-at-faults (s-a-f) at the checkpoints.
- See if you could bypass any test vector to have a minimum number of vectors to detect all the faults. State the reasons for bypassing the vectors.
- Submit all codes and reports on Moodle.
- This is a team assignment; each team(4 students per team) is assigned one circuit (kindly check the Moodle post for Question No.)
- **Deadline: 6<sup>th</sup> Oct 2022 11:59 PM**


1.




2.

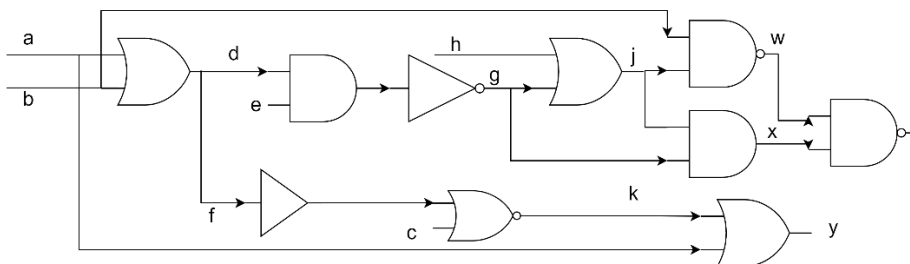


3.

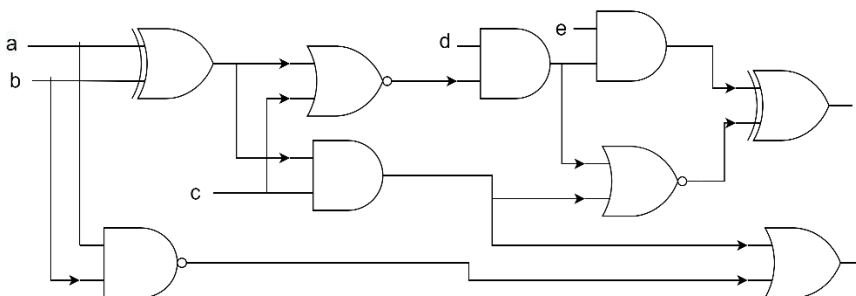


4.

 


5.

 

6.

 

7.

 

8.

